

Map-Fi Tag Receiver part


Leyan Zhu

Outline

- ▶ System Introduction
- ▶ My Task
- ▶ Envelope-demodulation Method
- ▶ Self-adaptive Envelop-demodulation Circuit
- ▶ Problems
- ▶ IC Design
- ▶ Q&A

System Introduction

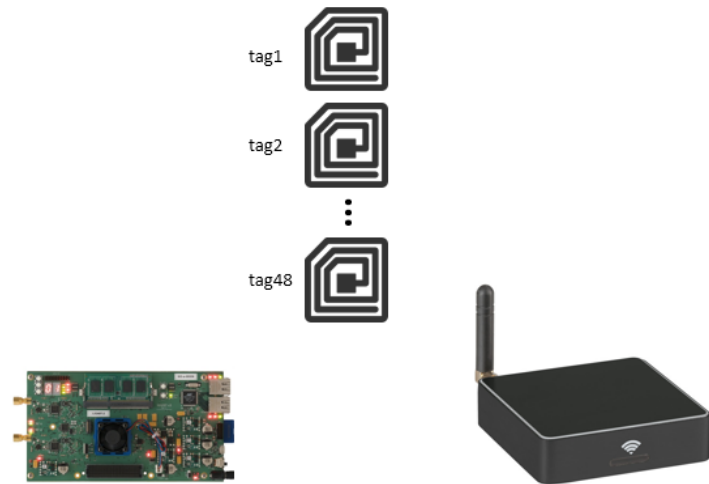Tags backscatter the provided RF signal to achieve low energy consumption communication



RF Transmitter : providing RF signal

Tag: backscattering to move the spectrum and imitate the 48 sub-channel of the OFDM system

Receiver : any device obeying 802.11g protocol

My Task


Design a PCB to receive the command sending to the Tag.
Command is used to synchronize and trigger.

Command signal:


2ASK modulation method

Carrier wave 2.4GHz

Data rate 250kbps


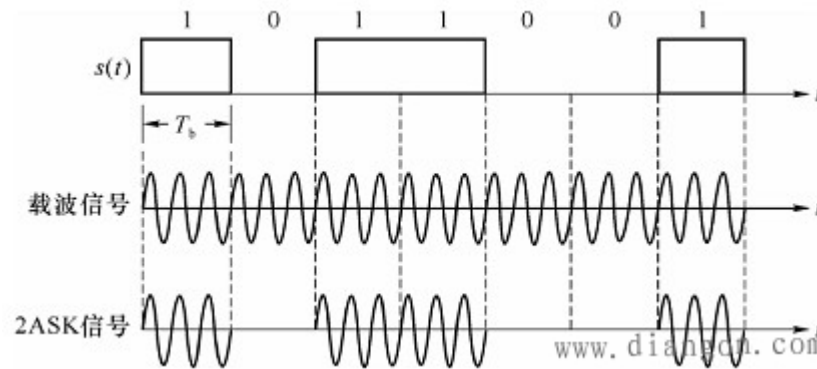


Envelope-demodulation Method

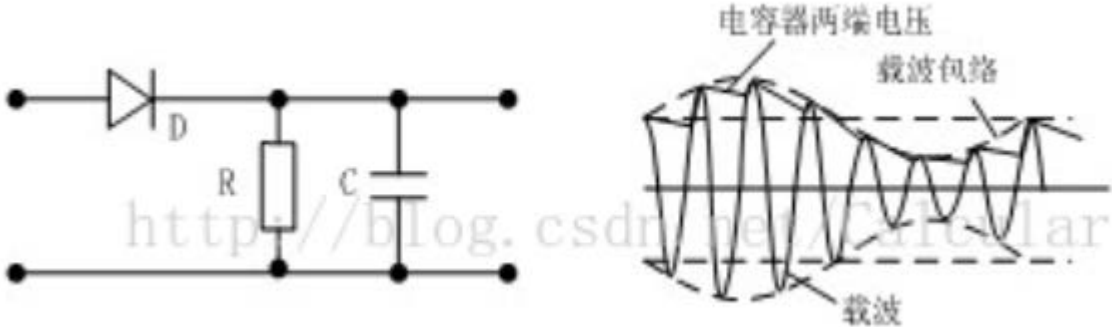

Typical Circuit


Using matlab

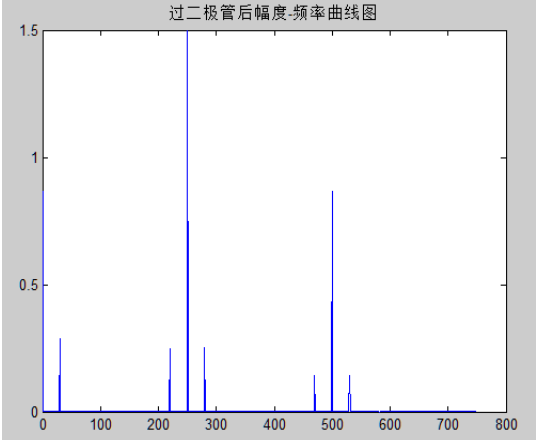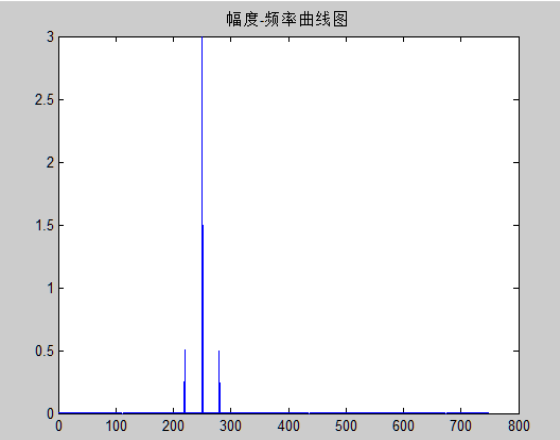

Diode Spectrum Analysis

Self-adaptive Envelop-demodulation Circuit

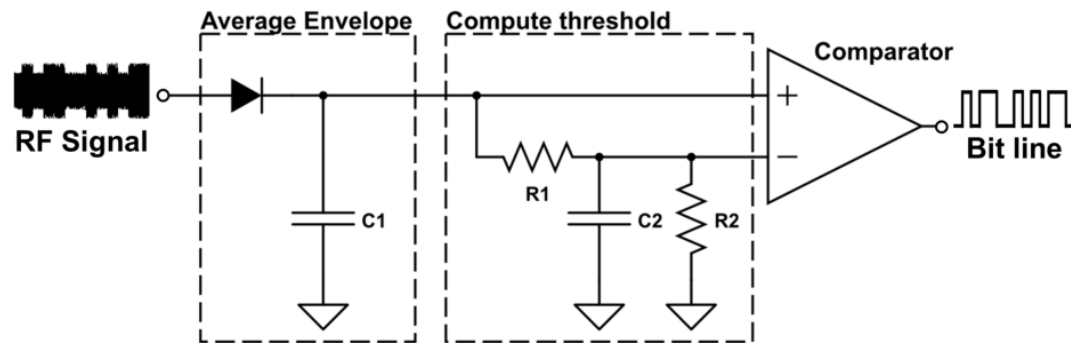
Problem: different transmission distance require different threshold



Solve the transmission distance problem

Threshold decided by the signal itself

My Design

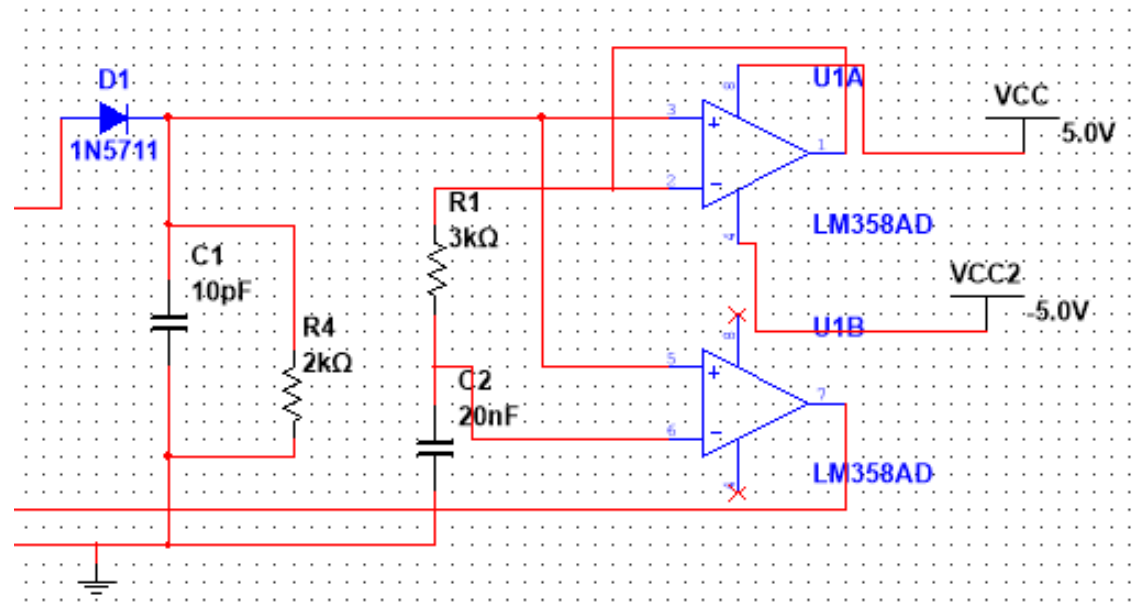

Part1: envelope-demodulation circuit

Part2: voltage follower

Part3: low pass fliter

Part4: comparator

Problems

1. Amplitude

-30dBm signal voltage 220mV

Germanium diode turn on voltage 0.2~0.4V

(now this is not a problem.....)



2. Frequency

Losing unilateral conduction characteristic

Special diode

IC Design

U1 LT5534 power detect component

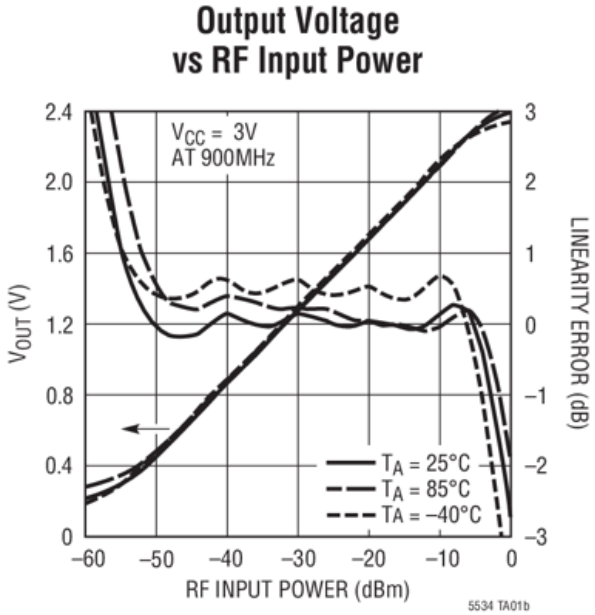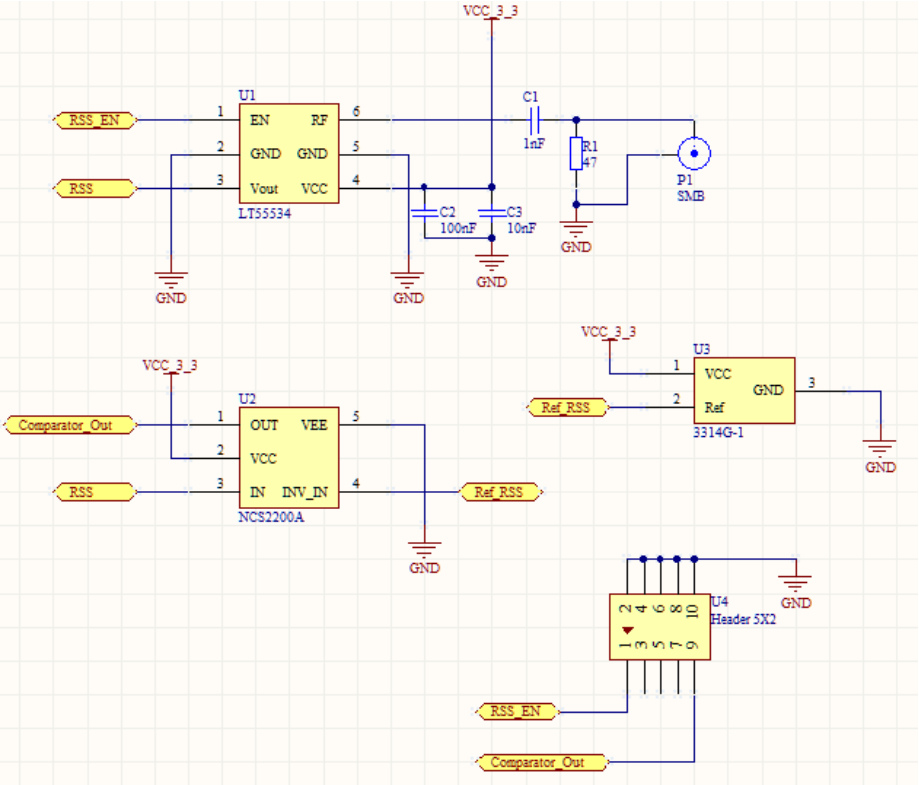

A bit high energy consumption

Q&A



Thank you!

The background features abstract, overlapping geometric shapes in various shades of green, ranging from light lime to dark forest green. These shapes are primarily located on the right side of the frame, with some extending towards the left. The overall aesthetic is clean and modern.